

**CEL 2 & ETL 2: Analog
and Digital Systems**

T005

**Friday, 01/11/2013
8:30 - 11:30 AM**

WORKFORCE DEVELOPMENT AUTHORITY



P.O.BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2013,
TECHNICAL AND PROFESSIONAL TRADES**

EXAM TITLE : Analog and Digital Systems

OPTIONS:

- **Computer Electronics (CEL)**
- **Electronics and Telecommunication (ETL)**

DURATION: 3hours

INSTRUCTIONS:

The paper contains **three (3)** sections :

Section I: Fourteen (14) questions, all Compulsory ;	55marks
Section II: Five (5) questions, Choose any three (3) ;	45marks
Section III: Three (3) questions, choose any ONE (1)	15marks

Section I: All the 14 questions are compulsory 55marks


01. Define the following terms : **3marks**
- Code converter
 - A flip-flop
 - Modulus of a counter

02. Minimize the following Boolean expressions by using karnaugh map (k.map).
 $F(W, X, Y, Z) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$


$$F = \overline{A}\overline{B}\overline{C} + \overline{B}C\overline{D} + A\overline{B}\overline{C} + \overline{A}BC\overline{D}$$

2marks

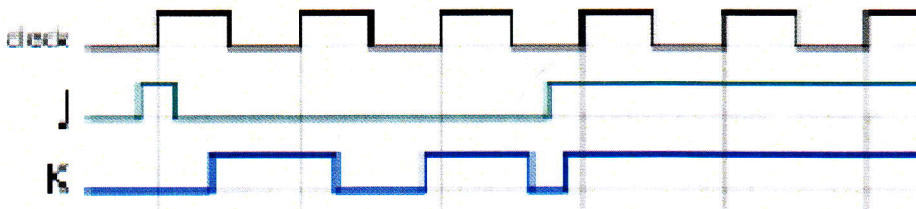
03. Learn the JK flip-flop waveform below and draw out the corresponding waveform of Q and \overline{Q} . Assume that at the initial the Q =0 (Low state). The clock signal is activated on High-to-Low transition. **2marks**



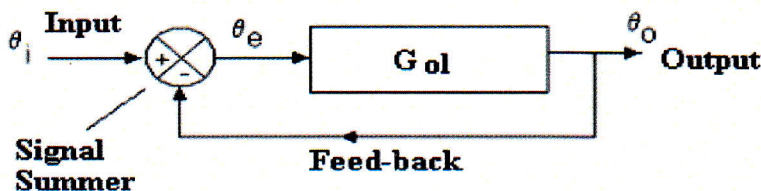04. Find out the transfer function of the closed loop control system below. **3marks**




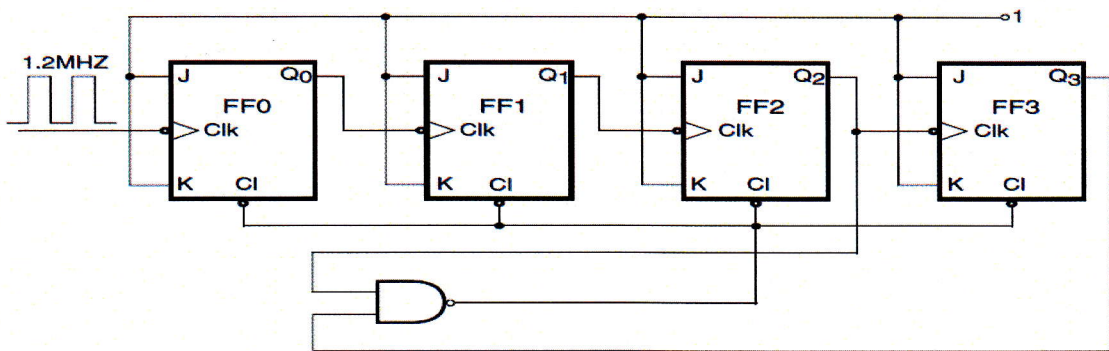05. Refer to the binary ripple counter of figure shown below; determine the modulus of the counter and also the frequency of the flip-flop Q3 output. **6marks**



06. What are the methods for obtaining sine wave output from an inverter? **5marks**
07. What are the main blocks of a switched mode power supply (SMPS)? **5marks**
08. Identify different types of inverters or DA-AC converters. **6marks**
09. Identify two (2) among different types of protection functions that a series-pass transistor voltage regulator can include. **2marks**
10. Identify different types of memories based on the way data access the memory. **4marks**
11. Consider a family of logic gates which operates under the static discipline with the following voltage thresholds: $V_{IL}=1.5V$; $V_{OL}=0.5V$; $V_{IH}=3.5V$ and $V_{OH}=4.4V$. Determine the noise margins. **6marks**
12. What are the two main difficulties of variable frequency system? **2marks**

13. Refer to this figure below,

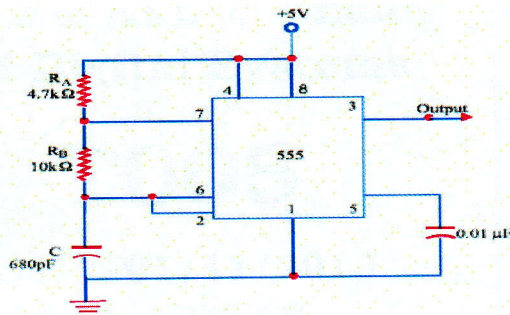

- Calculate:
- a) The Discharging time (T_{OFF})
 - b) The charging time (T_{ON})
 - c) The oscillation time (Period),
 - d) The oscillation frequency
 - e) The duty cycle


5marks

14. The speed of an electric motor is directly proportional to voltage such that $N=20V$ where V is Volts and N in rev/min. The motor is controlled by a power supply which has an output voltage related to the position of the control knob by $V=2\phi$ (in degrees). Draw the block diagram and deduce the overall transfer function. Determine the output speed when the knob is set to 60° .


4marks

Section II. Choose and answer any three (3) questions. 30marks

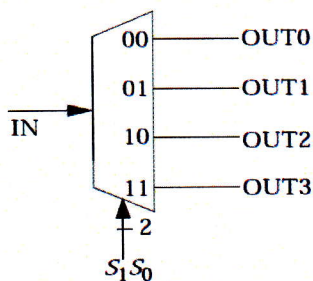
15. Clearly describe the working principle of 555 timers by using internal equivalent circuit **10marks**
16. a) Identify the main components of a programmable Logic Controller (PLC). **9marks**
 b) What is a Ladder Logic? **1mark**
17. Identify the function represented by the module shown below. Determine the Boolean expression of each output and implement it using only NAND gates. **10marks**



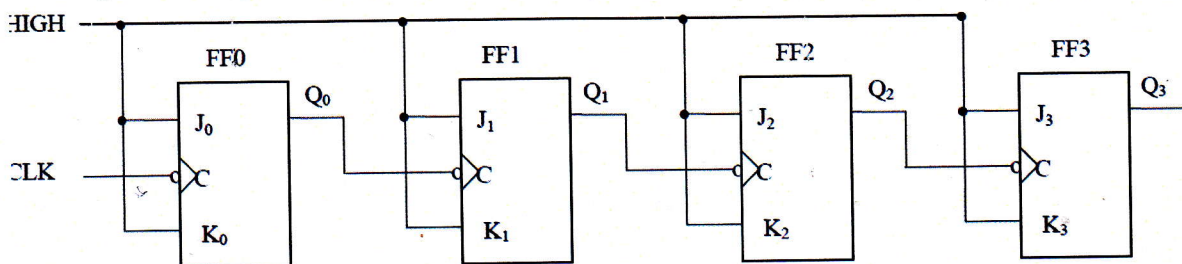
18. Consider the circuit shown below and answer to following questions : **10marks**
- a) What type of circuit is represented?
 - b) If each flip-flop has a propagation delay of 10ns, determine the total propagation delay time.
 - c) Determine the maximum frequency (in MHz) at which the circuit is operated.
 - d) Develop a timing diagram showing the Q output of each flip-flop.



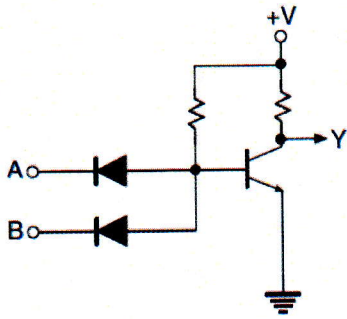19. a. Give the function performed by the following circuit. 1mark




b. Describe each part of the following SFC. 9marks

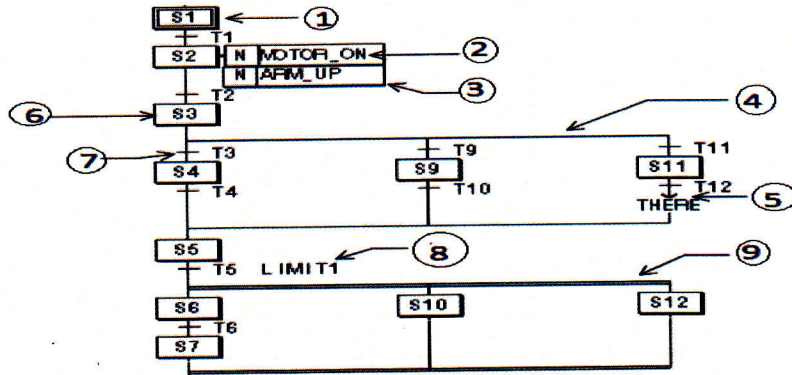

Section III. Choose and answer any one (1) question 15marks

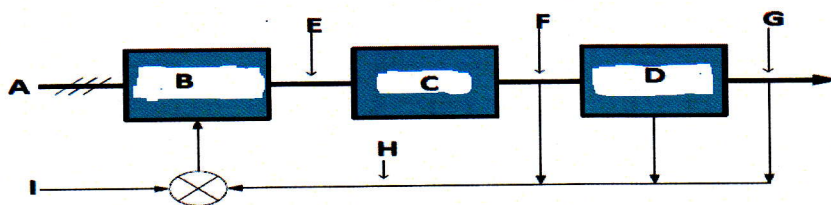20. The following is a block diagram of a typical pulse width modulation adjustable speed drive configuration of a motor; determine the function or variable type represented on the diagram by letters A, B, ..., I and specify the six (6) basic protections that must be performed on such circuit. 15marks



21. a. Describe the term PID in the automation control system and give its block and Transfer Characteristic. 8marks

b. In the automation system describe a PI block and give the Output Characteristics of it. 7marks

22. After analyzing and giving the function of the following ladder diagram, convert it into STL and FBD. 15marks

