

**MVM - Automotive Electricity and  
Electronics**

**T011**

**Monday, 04/11/2013**

**1:30 - 4:30 PM**

**WORKFORCE DEVELOPMENT AUTHORITY**



**P.O.BOX 2707 Kigali, Rwanda Tel: (+250) 255113365**

---

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2013,  
TECHNICAL AND PROFESSIONAL TRADES**

**EXAM TITLE: Automotive Electricity and Electronics**

**OPTION: Motor Vehicle Mechanics (MVM)**

**DURATION: 3hours**

**INSTRUCTIONS:**

The paper contains **Three (3)** Sections:

Section **I:** Eighteen (**18**) questions, **all Compulsory** **55marks**

Section **II:** Five (**5**) questions, Choose any **Three (3)** **30marks**

Section **III:** Two (**2**) questions, Choose any **One (1)** **15marks**

**Section I : Attempt all the 18 questions 55marks**

01. Define the following terms: **4marks**  
a) Insulator  
b) The electrical field  
c) Conductor  
d) Junction rule
02. What is the equipment used to measure the current in electrical circuit and how it can be connected? **2marks**
03. Show clearly with a simple sketch the relay including the diode. **2marks**
04. State at least four methods used to generate voltage. **2marks**
05. a) How many cells can have the battery of 12volts? **1mark**  
b) State four (4) electrical measurements that can be done often in electrical workshop. **2marks**
06. State four advantages of electronics components use. **2marks**
07. Write down in full the meaning of the following: **2marks**  
AFT, TPS, CKPS, WTS
08. a) Indicate with formulas the values of a)  $U_t$  b)  $I_t$  and c)  $R_t$  in a circuit having three resistances connected in series. **3marks**  
b) Give the unit for each value. **3marks**
09. Define the following:  
a) Inductor **1mark**  
b) Capacitor **1mark**
10. Using a sketch, show how to test the diode with ohmmeter. **3marks**
11. Sketch the symbols of transistors used in electronic circuits. **2marks**
12. What are the values of a Gasoline's engine ratios of Air-fuel mixture for the following conditions: **2marks**  
a) Cold engine starting; b) Idling engine;  
c) Part throttle opening; d) Full acceleration;
13. State four (4) applications of a transistor. **2marks**
14. A 9 volt battery supplies power to a cordless curling iron with a resistance of 18 ohms. Determine the current flowing through the curling iron. **2marks**
15. With net sketch of a closed electrical circuit show the way of move of electrons. **5marks**



16. Draw the electrical diagram of:

a) Alternating current;

b) Direct current;

**4marks**

17. Identify any safety precautions to be applied when you are performing battery maintenance. **5marks**


18. With sketches explain how electrolyte reacts chemically with leads plates during charging /discharging process. **5marks**

**Section II: Choose and Answer any Three (3) questions 30marks**

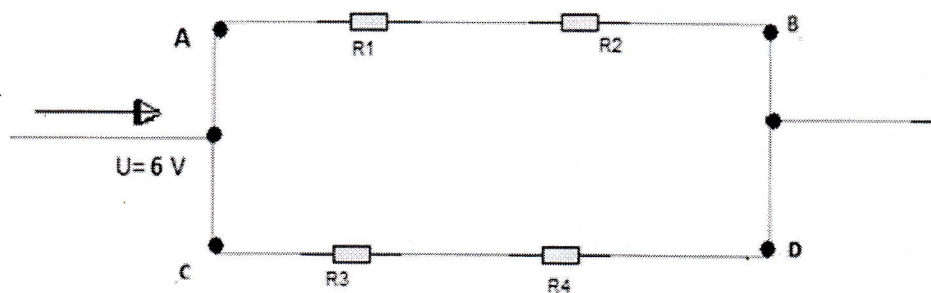19. In electrical circuit below the values of the resistances are the following: **10marks**

$$R_1=2 \Omega \quad R_2=1 \Omega \quad R_3=2.6 \Omega \quad R_4=4 \Omega$$

Calculate:  $R_T$ ,  $I_T$ , I of AB, I of CD,  $U_1, U_2, U_3, U_4$



20. a) State and distinguish with a net sketch between the internal alternator circuits. **9marks**

b) State two electrical behaviors of materials. **1mark**

21. Here are given some components used in electrical circuit: wires, simple relay, motor and switch;

a) Make a circuit in which a switch is opening. **4marks**

b) Draw the electronic circuit where the transistor is used as amplifier. **6marks**

22. Here below are given electrical components: voltage generator relay, wires, two horns and horn's switch;

a) Draw a circuit diagram in which a relay is closing. **5marks**

b) List five(5) basic electrical workshop rules. **5marks**

23. a) List five (5) physical health symptoms to be observed if serious contact with hazardous materials while working in an electrical workshop. **5marks**

b) Give five (5) reasons of spark missing at all speed and their solutions. **5marks**

**Section III: Choose and Answer any One (1)question 15marks**

**24. a)** What are the five basic types of the computer gates? **10marks**

**b)** List ten possible causes and remedies of an alternator which does not supply the electrical consumers with energy and not charges the starter battery. **5marks**


**25. a)** The values of resistances in an electrical circuit below are:

$$R_1=1\Omega, R_2=2\Omega, R_3=2\Omega, R_4=1\Omega, R_5=1.4\Omega, R_6=5\Omega, R_7=2.6\Omega,$$

$$R_8=1.3\Omega, R_9=2\Omega$$

Calculate:  $I_T, U$  of BC, EG, 5, 6, 8 and 9

**14marks**

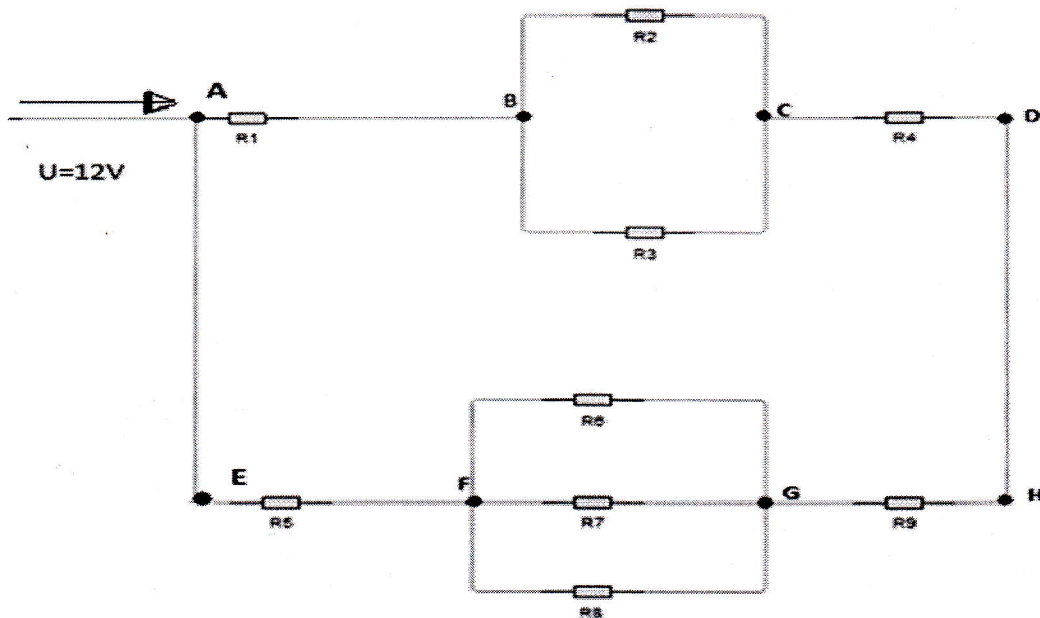

**b)** State the ways of heat transmission.

**1mark**