

ELC – Electrical Technology

T039

Tuesday, 04/11/2014

8:30 - 11:30 AM

WORKFORCE DEVELOPMENT AUTHORITY



P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2014
TECHNICAL AND PROFESSIONAL TRADES**

EXAM TITLE: ELT – Electrical Technology

OPTION: ELECTRICITY (ELC)

DURATION: 3hours

INSTRUCTIONS:

The paper is composed of **three (3) main Sections:**

Section I: Fifteen **(15)** questions, all **Compulsory**. **55marks**

Section II: Five **(5)** questions, **Choose any Three (3)**. **30marks**

Section III: Three **(3)** questions, **Choose any One (1)**. **15marks**

SECTION I. FIFTEEN (15) COMPULSORY QUESTIONS.

Energy
Time

01. Give three (3) reasons why alternating current (a.c) is used in the generation and transmission of electronic power. **3marks**


02. When does an electrical shock occur? **3marks**

03. An alternating voltage (a.v) is given by $12\sin 50$ Calculate the r.m.s and draw the wave form. **6marks**

04. Draw a line diagram of a manual switch with overload protection and a float switch controlling a pump motor for "pump" operation. **4marks**

05. For an R-L series a.c circuit, draw:

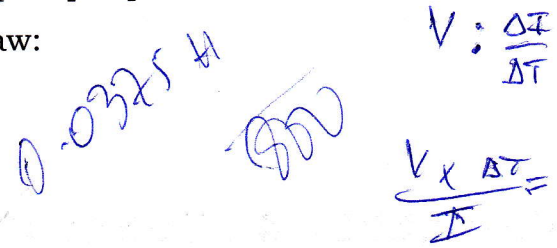- (a) a circuit diagram
- (b) phasor diagram
- (c) voltage diagram
- (d) impedance diagram.




4marks

06. A 6V battery is connected in series with 20Ω , 15Ω and 25Ω resistors. Find the voltage flowing in each resistor **2marks**

07. Define the following expressions:

- a) A motor starter.
- b) A contactor.

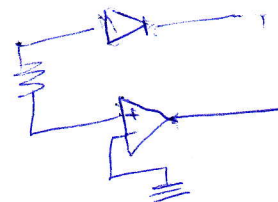

4marks

08. Differentiate conductors from insulators. **4marks**

09. Draw a well labeled circuit diagram for an inverting amplifier. **6marks**

10. What are the three different types of magnetic contactors? **3marks**

11. A current through a coil increases from 20A to 60A in 0.05 seconds and an e.m.f (e) of 30V is induced. Find the inductance of the coil. **3marks**

12. Where can a differential compound d.c motor be used? **2marks**

13. A factory has a 240-V supply from which the following loads are taken :


Lighting: Three hundred 150-W lamps, four hundred 100 W lamps and five hundred 60-W lamps

Heating: 100 kW

Motors: A total of 44.76 kW with an average efficiency of 75 percent

Misc. : Various load taking a current of 40 A.

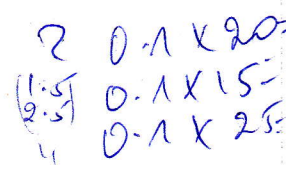Assuming that the lighting load is on for a period of 7hours /day, the heating for 16hours per day and the remainder for 3hours /day, calculate the weekly consumption of the factory in kWh when working on a 7-day week. **5marks**



14. According to the way the primary and the secondary windings are placed around the core, explain the types of transformers. **3marks**

15. Mention three (3) things that you can do as technician to maintain tools and electrical equipments in good conditions. **3marks**

SECTION II. ATTEMPT ANY THREE (3) QUESTIONS.

16. A coil of resistance 8 and inductance 140mH in series with a 150 capacitor is connected to a 240V, 50Hz supply.

Calculate:

- (a) the current flowing
- (b) the phase difference between the supply voltage and current;
- (c) the voltage across the coil
- (d) the voltage across the capacitor

10marks

17. Using sketches show how a field rheostat or armature rheostat could be used to adjust the speed of a dc shunt motor.

10marks

18. (a) With the aid of a labeled circuit diagram, explain how an earth electrode is installed

6marks

(b) Give and explain any two (2) applications of earthing.

4marks

19. a) Classify AC motors according to their principle of operation.

5marks

b) Describe a d.c generator.

5marks

20. Use Kirchhoff's law to determine the currents flowing in each branch of the network shown in figure1 below:

10marks

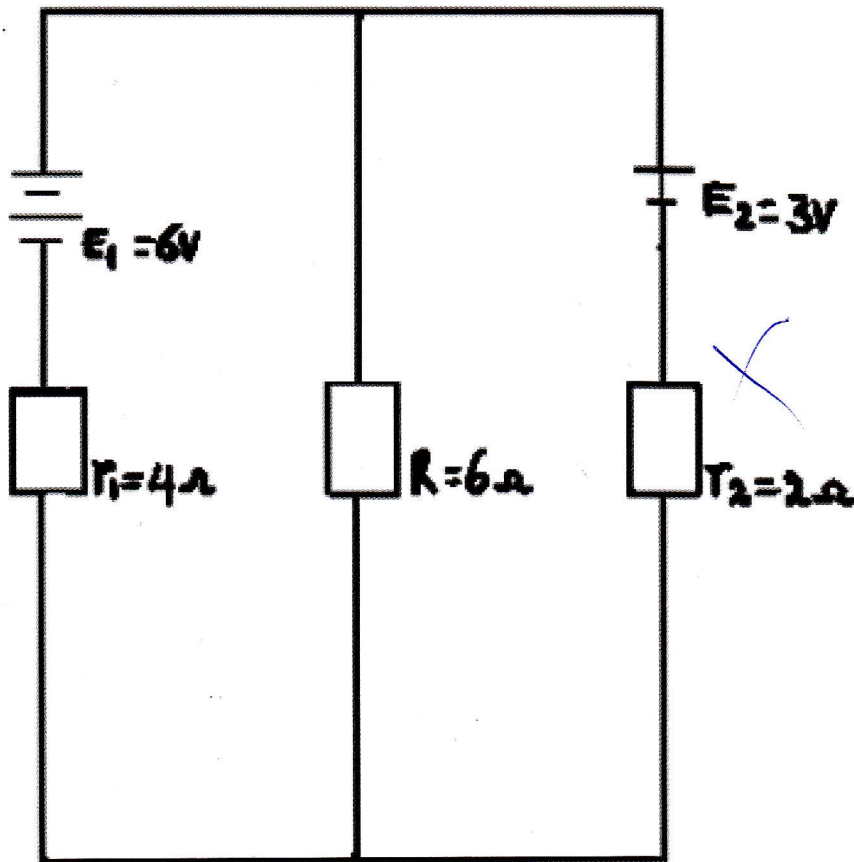


Fig. 1

0-0471

STEP UP / STEP DOWN

10/10

$R^2 + (Lw)$

SECTION III. ATTEMPT ANY ONE (1) QUESTION.

21. a) Make classification of all losses which take place in a DC generator.
- b) A 4-pole, Lap-connected d.c. machine has an armature resistance of 0.15 ohm. What will be the armature resistance of the machine if it is rewound for wave-connection? Justify by connections diagrams. **15marks**
22. Two batteries, each of e.m.f 10V and internal resistance 0.5Ω are connected in:
- (i) series ; (ii) parallel to supply a load which has a resistance of 4Ω .
- (a) make circuit diagrams of these circuit connections. **6marks**
- (b) calculate the current and voltage across the load in each case. **9marks**
23. Draw and explain the autotransformer starting circuits. **15marks**

Handwritten notes in blue ink on the right side of the page, including a large '60' and some illegible scribbles.